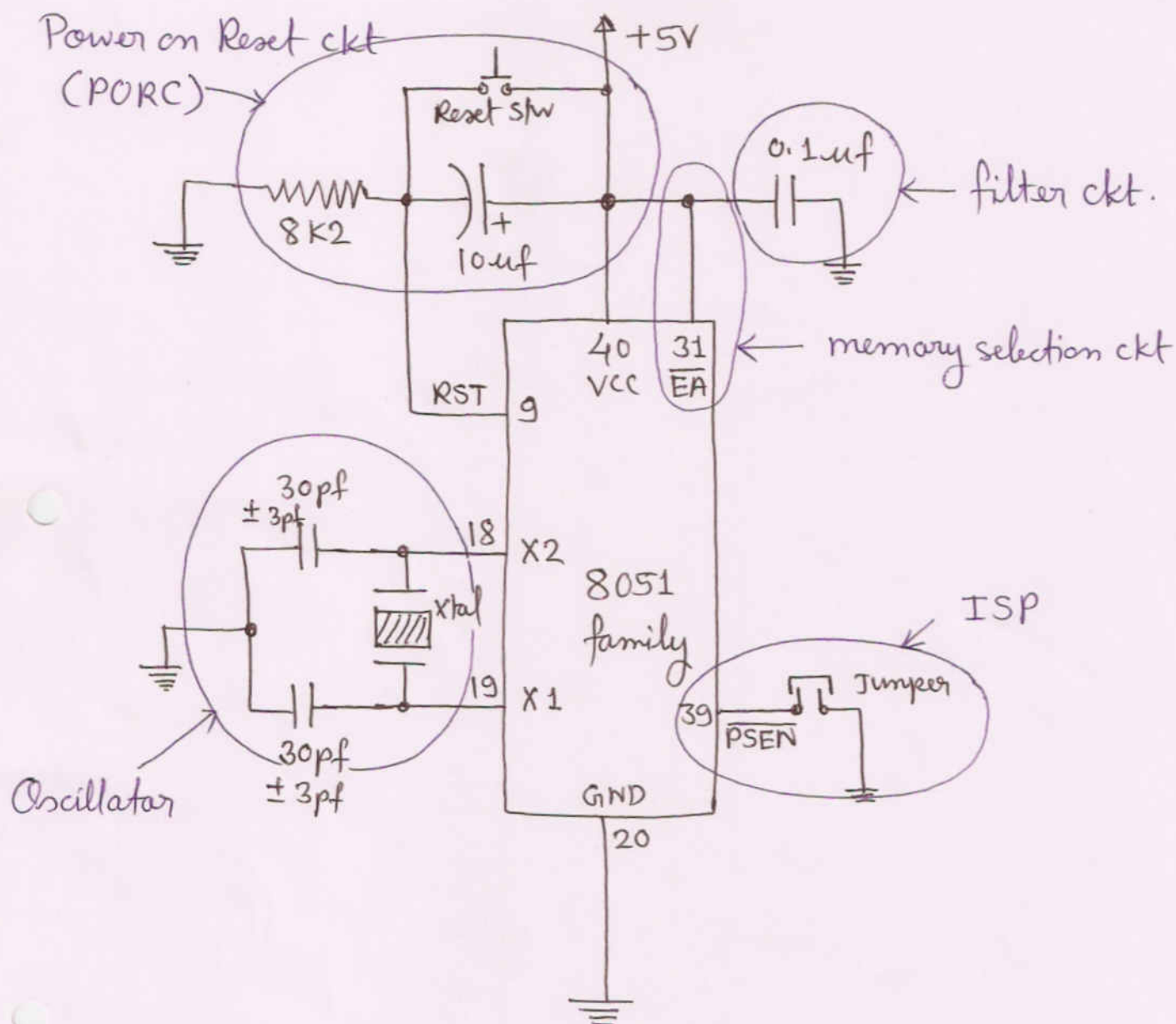


## Basic Circuit Diagram of $\mu C$ :-



the above is the minimum system configuration that is required for a  $\mu C$  to start or to run properly. this the common circuit for any  $\mu C$  based embedded system. It has five basic blocks —


- ① filter circuit unit
- ② Xtal Oscillator circuit unit
- ③ Power on Reset circuit unit
- ④ Code memory selection unit
- ⑤ In System Programming unit.

### ① Filter Circuit Unit :-

the job of this circuit is to filter out any A.C. signal noise present in the power supply input. The  $\mu C$  requires pure D.C. volts (+5V) for its proper working. For this purpose we have connected a  $1\mu f$  capacitor between pin 40 of  $\mu C$  & ground. Capacitor have basic function of passing A.C. signal from it & blocking D.C. signal, because the impedance of capacitor is given by -  $X_c = \frac{1}{2\pi f_c}$ .

Q. The filter capacitor is also included in the power supply system, even though it is mandatory to connect it very near to pin no 40 of  $\mu C$  - why?

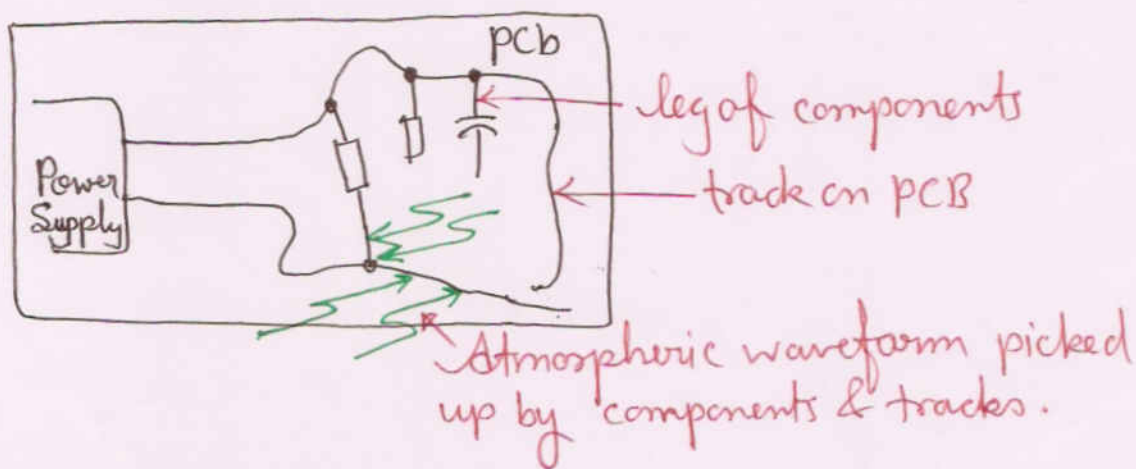
A. To answer this question first we will see how the A.C. noise is generated even though there is already filter circuit in the power supply system - there are various frequencies present in the atmosphere which continuously collide with the track of the PCB & the open legs of the various components mounted on it. Due to this flow of electrons are disturbed producing small waveform in the circuit. this is known as Component noise or Atmospheric noise.





this is the reason that again noise (A.c. signals) are induced in the circuit even there are several filter circuits in the power supply section.

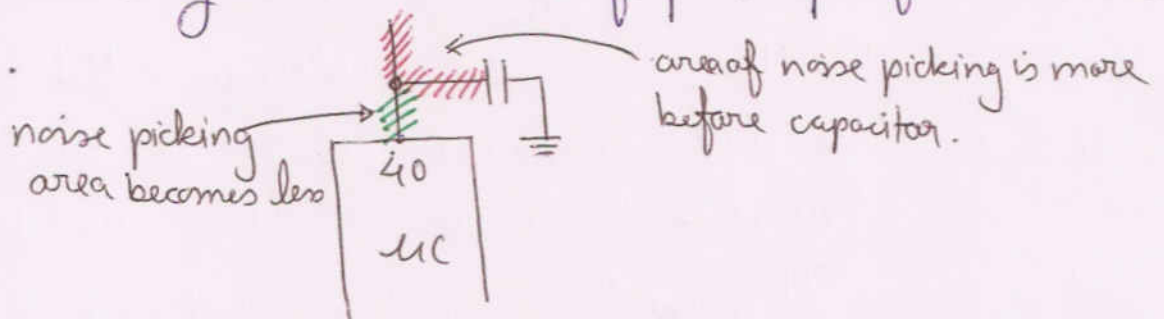
By connecting  $0.1 \mu\text{f}$  capacitor very near to pin no 40 (i.e. near to VCC of  $\mu\text{C}$ ) makes it sure that all the component noise are reduced or filtered out and hence forth only pure D.C. will enter in  $\mu\text{C}$ . The noise entering to  $\mu\text{C}$  becomes very less as area of pickup of noise becomes very less.



{ In any embedded system we will find a filter cap. near to each digital IC - as recommended by datasheets. }
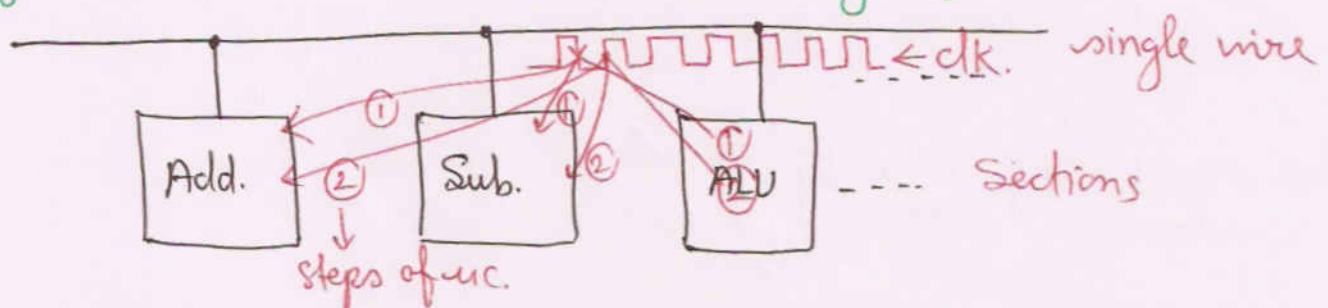
## ② Xtal Oscillator circuit Unit :-

the  $\mu\text{C}$  is internally made up of different blocks or individual sections. To synchronize the various operations of various sections in  $\mu\text{C}$  it requires a common clk pulse to be run. this is provided by the external Xtal connected. the operations are carried out at -ve going edge trigger  $\downarrow$  of the pulses simultaneously by each sections.



Thus the speed of  $\mu C$  depends upon the frequency of the  $clk$  pulse. The external  $clk$  is divided internally by 12 in case of standard 8051 family  $\mu C$ . We can connect 0-24 MHz crystal according to datasheet. The capacitors are used to support the crystal for oscillations and values are standard according to datasheet ( $30\text{ pf} \pm 3\text{ pf}$ ).

Q. What is standard Crystal?

A. Any Crystal value that is multiple of divider value of  $\mu C$  is standard crystal. Thus 12 MHz crystal is generally assumed as standard crystal for 8051.

Q. If 12 MHz crystal is standard crystal then why we use 11.0592 MHz crystal in most of embedded systems?

A. 11.0592 MHz crystal is generally used in communication based system where  $\mu C$  needs to communicate with its UART (i.e. serial port - universal asynchronous receive & transmit). For serial communication  $\mu C$  needs to generate one of the following standard baud rates -

110 bps  
300 bps  
1200 bps  
2400 bps  
4800 bps  
9600 bps  
⋮  
115200 bps.

{ def. of baud rate:- total no. of bits passing through any cross section of a conductor in one second is known as baud rate. it is measured as bps. i.e. bits per second.




the formula to generate baudrate is given by the following equation —

$$\text{Reload Value} = 256 - \text{Abs}(((\text{crystal } f^n / 12) / 32) / \text{baud Rate})$$

here crystal is part of it. if we substitute 12MHz crystal value in the equation then the reload value of timer will not be an integer data for all the standard baud rates. 11.0592 MHz crystal generate exact baud rate values which is very important in any com<sup>n</sup> system otherwise data will be garbage at the receiver end.

Q. In which Type of embedded system 12MHz crystal is used?

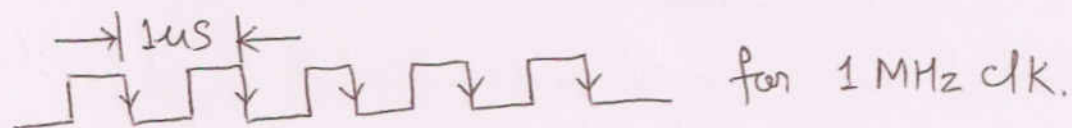A. 12MHz crystal is used in timebased application where we require exact time delays. In  $\mu\text{C}$  12MHz value is divided by 12 producing 1MHz clk pulse. the time between successive -ve going edge trigger is  $\nabla$  1  $\mu\text{s}$ .



thus to generate specific time delay (say 100  $\mu\text{s}$ ) just count that many no of pulses (100 pulses) and we will get that.

---

thus —

for time based App<sup>n</sup> — 12MHz


for Com<sup>n</sup> based App<sup>n</sup> — 11.0592MHz.

### ③ Power On Reset Circuit :-


Reset circuit is generally used to restart the code execution process of  $\mu C$  from the starting code mem. location (i.e.  $0000h$ ) in case of hanging.

to reset  $\mu C$  we need to apply high logic to the pin no 9 (i.e. RST-Reset). When it is held for nearly two machine cycles while oscillator is running resets the controller.

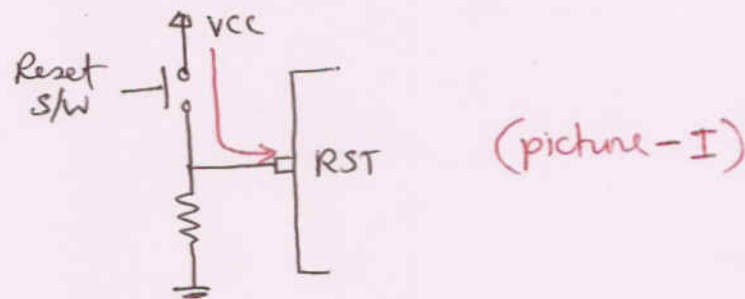
To achieve this we can use a simple ckt like following—



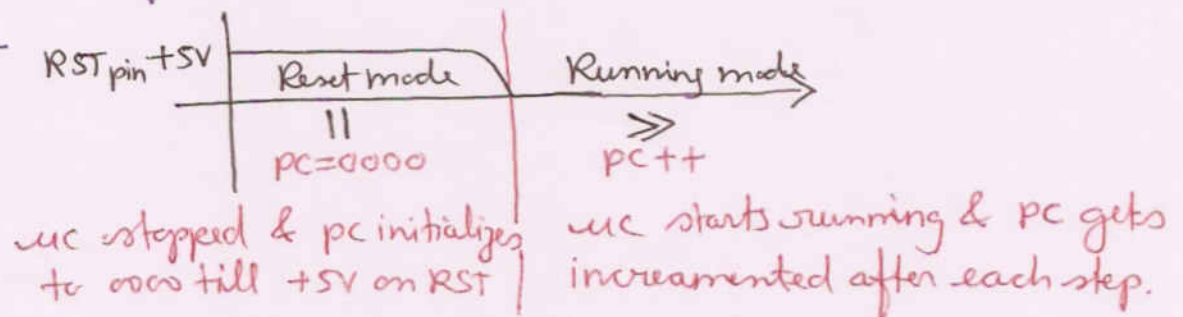in the above circuit when the switch is pressed momentarily VCC goes to the reset pin & controller goes in reset mode till the switch is pressed. thus the behaviour can be shown as—



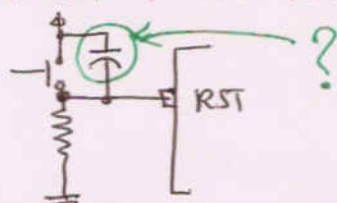
Q. When we can achieve Reset condition of  $\mu C$  just by using the above picture-I circuit; Why the  $10\mu f$  capacitor is connected in P.O.R.C.? What is its use?





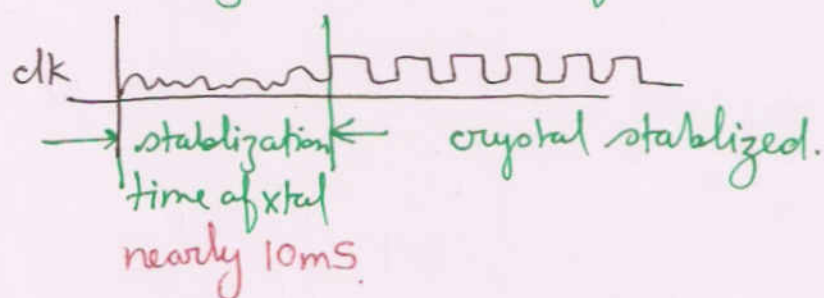
A. the reason to use capacitor have relation with the xtal oscillations connected  $\rightarrow$

When we switch on the power supply, voltage immediately raises from 0 to +5V. the crystal is a device that takes some time to get initialized. It gets vibrated or becomes unstable initially, after some time its oscillations are stabilized.  $\rightarrow$  this time is known as stabilization time of xtal.



if the uc starts fetching instructions when the crystal is unstable, it will start misbehaving & will get hanged as the clk to all its sections are not proper & synchronization will not occur. So as to avoid this situation we introduce a capacitor between VCC & RST pin.

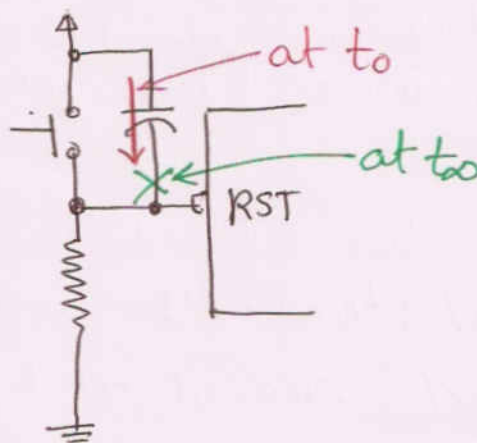the capacitor have properties like - initially short circuit & finally open circuit.



so as soon as the power is applied to the system, cap.

gives a path for D.C. current to RST pin which forces controller to go in reset mode. (i.e. controller does not fetch instructions). After some time when capacitor is charged it acts like an open circuit for D.C. current and  $\mu C$  pin RST is by default connected to GND via resistor producing logic low on pin. Now the  $\mu C$  starts fetching instructions.

the charging of capacitor takes more time than stabilization of xtal and it is given by formula—  
$$\text{time} = R \times C$$

this time is also known as RC time constant or Reset timing of  $\mu C$ . in our circuit it is —  
$$82\text{ms} = 8.2\text{K} \times 10\mu$$

thus  $\rightarrow$  when we switch on power supply  $\mu C$  gets started after 82ms.

$\rightarrow$  crystal takes approx. 10ms to get stabilized.

$\rightarrow$  it is guaranteed that  $\mu C$  will never hang & will start properly whenever we switch on the power supply.


Q. Why this circuit is known a Power on Reset Circuit & not only reset circuit ?

A. Since the capacitor comes in picture only when we start power supply it is known as PORC. after this capacitor has no use.



Q. What is the waveform at the time of POR.

A.

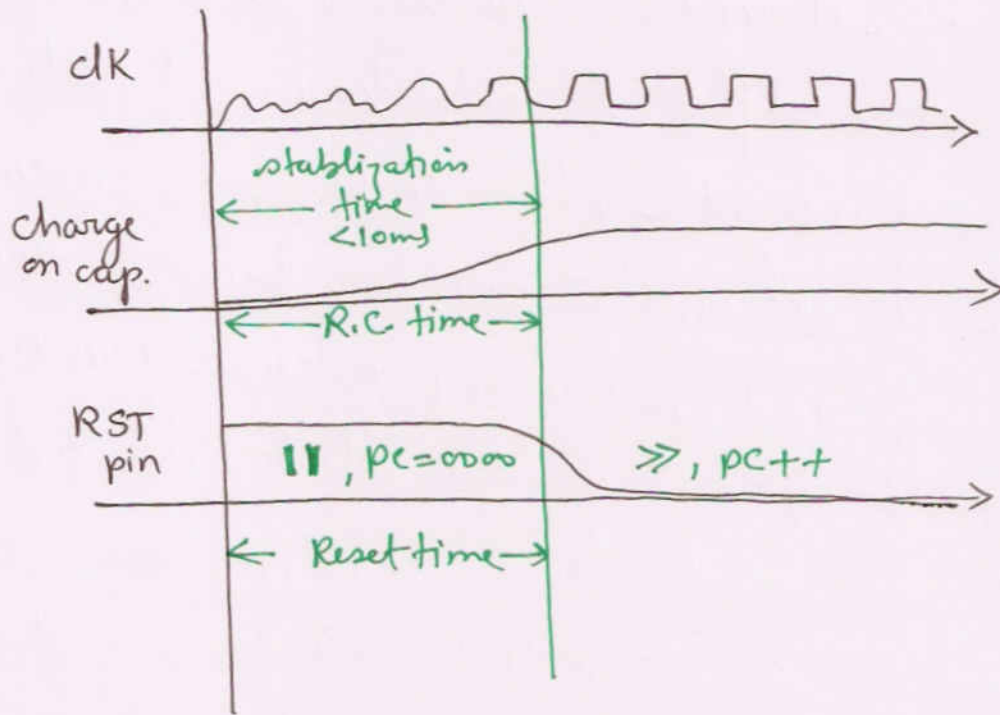

Q. What is the reset timing of the Project?

A. Reset timing of project is nothing but the RC time constant. it is 82ms in our case. according to datasheet it should be always greater than 10ms.

Reset timing indicates time delay between power supply switching & actual execution of system.

#### ④ Code Memory Selection Unit :-

this circuit connectivity tells  $\mu C$  whether to fetch instructions from internal code memory or from external code memory. When our code size is more than the  $\mu C$  code mem. capacity then we interface external code memory to the system & the instructions are stored in that. The  $\overline{EA}$  (external Access bar)

should be connected to GND in this case. As we are not using external instruction memory, we have connected it to VCC.


### ⑤ In System Programming setting (I<sub>0</sub>S<sub>0</sub>P<sub>0</sub>) :-

PSEN (program store enable bar) is used to toggle  $\mu C$  in programming mode. when we connect this pin to GND & then switch on the power supply then the controller is in programming mode & no instructions are being executed. In this mode we can connect the  $\mu C$  with PC-serial port (RS-232) and code can be downloaded in it. In system Programming is generally used in P89C51RD2BN controller.

---

Extra :-

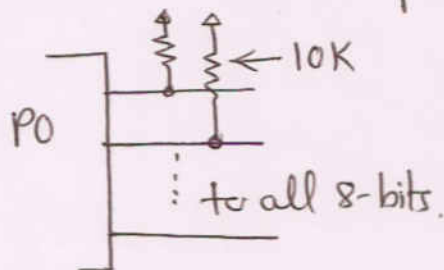Sometime we connect pull resistors to  $\mu C$  port 0.



this pull resistors are known as Resistor N/w of 10K. the job of these resistors are to increase the voltage (pull-up) of port 0 as they are weak by nature. they provides only 1.7 volts as they have no internal pull-ups. and are open-drain port.